

Basic Logic Design with Verilog

TA: Chihhao Chao

chihhao@access.ee.ntu.edu.tw

Lecture note ver.1 by *Chen-han Tsai*
ver.2 revised by *Chih-hao Chao*

Lecture Note on Verilog, Course #90132300, EE, NTU, C.H. Chao

Outline


- Introduction to HDL/ Verilog
- Gate Level Modeling
- Behavioral Level Modeling
- Test bench
- Summary and Notes

Introduction to HDL/ Verilog

What is HDL/Verilog


- Why use HDL (Hardware Description Language)?
 - Design abstraction: HDL \longleftrightarrow layout by human
 - Hardware modeling
 - Reduce cost and time to design hardware
- Verilog is one of the most popular HDLs
 - VHDL (another popular HDL)
- Key features of Verilog
 - Supports various levels of abstraction
 - Behavior level
 - Register transfer level
 - Gate level
 - Switch level
 - Simulate design functions

Hardware Design Flow

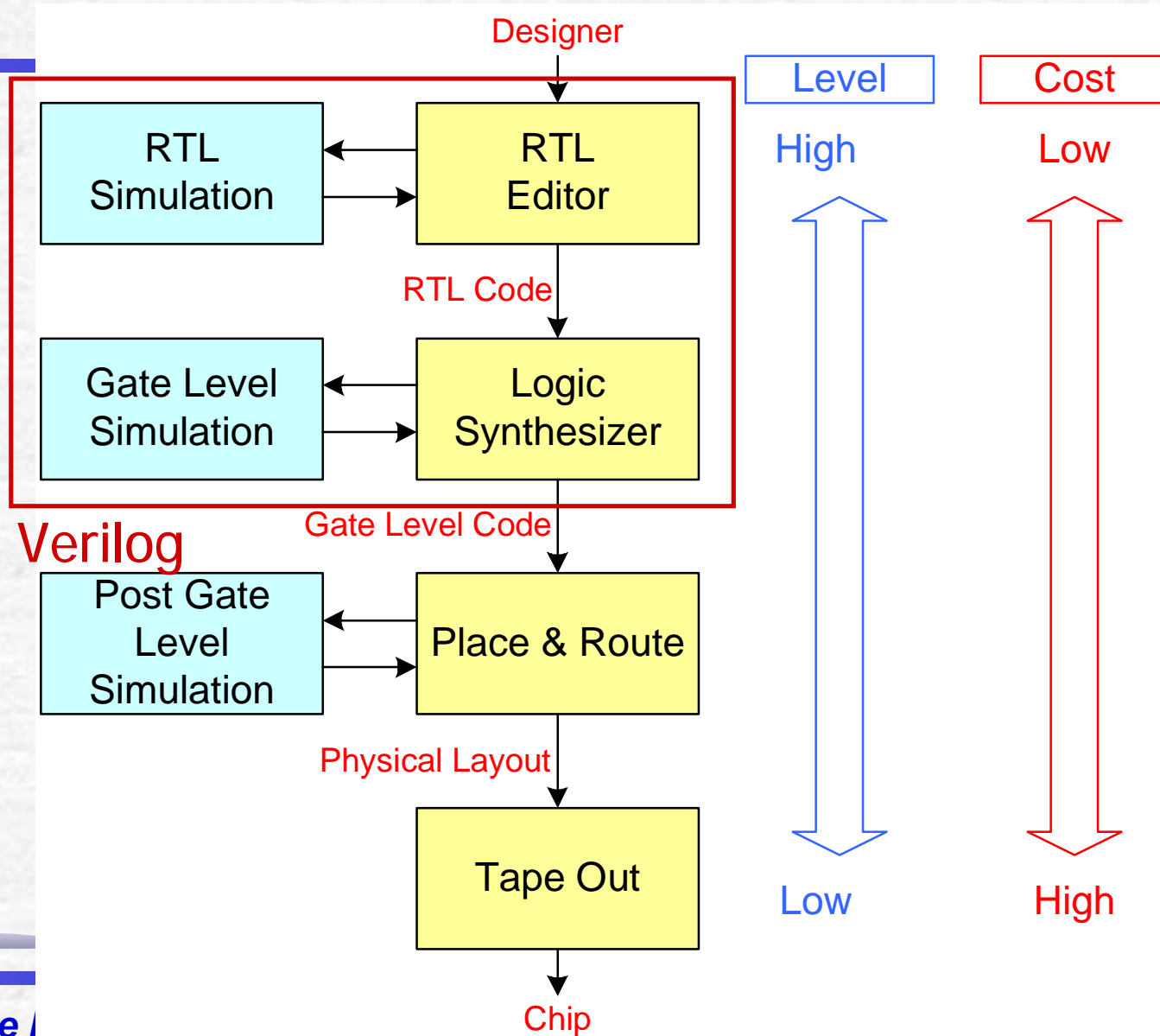

An Example

1-bit Multiplexer

 


```
if (sel==0)
    out = in1;
else
    out = in2;
```

sel	in1	in2	out
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$$\text{out} = (\text{sel}' \cdot \text{in1}) + (\text{sel} \cdot \text{in2})$$

Gate Level Description

 

```
module mux2(out,in1,in2,sel);  
    output out;  
    input in1,in2,sel;  
  
    and a1(a1_o,in1,sel);  
    not n1(iv_sel,sel);  
    and a2(a2_o,in2,iv_sel);  
    or o1(out,a1_o,a2_o);  
endmodule
```

Gate Level: you see only netlist (gates and wires) in the code

Behavioral Level/RTL Description

```
module mux2(out,in1,in2,sel);
  output out;
  input in1,in2,sel;
  reg out;

  always@(in1 or in2 or sel)
  begin
    if(sel) out=in1;
    else out=in2;
  end
endmodule
```

```
module mux2(out,in1,in2,sel);
  output out;
  input in1,in2,sel;

  assign out=sel?in1:in2;
endmodule
```

always block


assign

RTL: you may see high level behavior in the code

Behavior: event-driven behavior description construct

Verilog HDL Syntax

A Simple Verilog Code

 

Module

- Basic building block in Verilog.
- Module
 1. Created by “declaration” (can’t be nested)
 2. Used by “instantiation”
- Interface is defined by ports
- ⊖ May contain instances of other modules
- ⊖ All modules run concurrently

Instances


- A module provides a template from which you can create actual objects.
- When a module is invoked, Verilog creates a unique object from the template.
- Each object has its own name, variables, parameters and I/O interface.

Module Instantiation

```
module adder(out,in1,in2);  
    output out;  
    input in1,in2,sel;  
  
    assign out=in1 + in2;  
endmodule
```

instance
example
 
```
module adder_tree (out0,out1,in1,in2,in3,in4);  
    output out0,out1;  
    input in1,in2,in3,in4;  
  
    adder add_0 (out0,in1,in2);  
    adder add_1 (out1,in3,in4);  
endmodule
```



Analogy: module ↔ class

As *module* is to *Verilog HDL*, so *class* is to *C++ programming language*.

Format	<code>module m_Name(IO list);</code> ... <code>endmodule</code>	<code>class c_Name {</code> ... <code>};</code>
Instantiation	<code>m_Name ins_name (port connection list);</code>	<code>c_Name obj_name;</code>
Member	<code>ins_name.member_signal</code>	<code>obj_name.member_data</code>
Hierarchy	<code>instance.sub_instance.me mber_signal</code>	<code>object.sub_object.member_ data</code>

Analogy: module \leftrightarrow class

```
class c_AND_gate {  
  bool in_a;  
  bool in_b;  
  bool out;  
  void evalutate() { out = in_a && in_b; }  
};
```

Model AND gate with C++

```
module m_AND_gate ( in_a, in_b, out );  
  input  in_a;  
  input  in_b;  
  output out;  
  assign out = in_a & in_b;  
endmodule
```

Model AND gate with Verilog HDL

✎ **assign** and **evaluate()** is simulated/called
at each $T_{i+1} = T_i + t_{\text{resolution}}$

Port Connection

```
module FA1 (CO,S,A,B,CI);  
    output CO,S;  
    input  A,B,CI;  
  
    assign {CO,S} = A+B+CI;  
endmodule
```

- Connect module port by order list
 - FA1 fa1(c_o, sum, a, b, c_i);
- Not fully connected
 - FA1 fa3(c_o,, a, b, c_i);
- Connect module port by name *.PortName(NetName)*
 - FA1 fa2(.A(a), .B(b), .CO(c_o),.CI(c_i), .S(sum));
 - Recommended

Verilog Language Rule

- Case sensitive
- Identifiers:
 - Digits 0...9
 - Underscore _
 - Upper and lower case letters from the alphabet

```
/* Verilog HDL module
   Half adder
*/
module adder (out0,in1,in2);
    output [1:0] out0;
    input      in1,in2;

    assign out0 = in1 + in2
endmodule //end of module
```

- Terminate statement/declaration with semicolon “;”
- Comments:
 - Single line: // it's a single line comment example
 - Multi-line: /* when the comment exceeds single line, multiline comment is necessary*/

Register and Net

Registers

- Keyword : **reg**, integer, time, real
- Event-driven modeling
- Storage element (modeling sequential circuit)
- Assignment in “always” block

Nets

- Keyword : **wire**, wand, wor, tri
triand, trior, supply0, supply1
- Doesn't store value, just a connection
- input, output, inout are default “wire”
- Can't appear in “always” block assignment

Four-valued Logic


Verilog's nets and registers hold four-valued data

- 0 represent a logic zero or false condition
- 1 represent a logic zero or false condition
- Z
 - Output of an undriven tri-state driver – high-impedance value
 - Models case where nothing is setting a wire's value
- X
 - Models when the simulator can't decide the value – uninitialized or unknown logic value
 - Initial state of registers
 - When a wire is being driven to 0 and 1 simultaneously
 - Output of a gate with z inputs

Logic System

- Four values: 0, 1, x or X, z or Z // Not case sensitive here
 - The logic value x denotes an unknown (ambiguous) value
 - The logic value z denotes a high impedance
- Primitives have built-in logic
- Simulators describe 4-value logic (see Appendix A in text)

	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

 

Number Representation

Format: `<size>'<base_format><number>`

- `<size>` - decimal specification of number of bits
 - default is unsized and machine-dependent but at least 32 bits
- `<base format>` - ' followed by arithmetic base of number
 - `<d> <D>` - decimal - default if no `<base_format>` given
 - `<h> <H>` - hexadecimal
 - `<o> <O>` - octal
 - ` ` - binary
- `<number>` - value given in base of `<base_format>`
 - `_` can be used for reading clarity
 - `x, z` is automatically extended

Number Representation

Examples:

- `6'b010_111` gives `010111`
- `8'b0110` gives `00000110`
- `4'bx01` gives `xx01`
- `16'H3AB` gives `0000001110101011`
- `24` gives `0...0011000`
- `5'O36` gives `11110`
- `16'Hx` gives `xxxxxxxxxxxxxxxxxx`
- `8'hz` gives `zzzzzzzz`

Value and Number Expressions :

Examples

```
659          // unsized decimal
'h 837ff     // unsized hexadecimal
'o7460       // unsized octal
4af          // illegal syntax
4'b1001      // 4-bit binary
5'D 3        // 5-bit decimal
3'b01x       // 3-bit number with
               unknown LSB
12'hx        // 12-bit unknown
8'd -6       // illegal syntax
-8'd 6       // phrase as - (8'd6)
```

// underline usage


```
27_195_000
16'b0001_0101_0001_1111
32'h12ab_f001
```

// X and Z is sign-extended

```
reg [11:0] a;
initial
begin
    a = 'hx;          // yields xxx
    a = 'h3x;         // yields 03x
    a = 'h0x;         // yields 00x
end
```


Net Concatenations :

An Easy Way to Group Nets

 

Representations

Meanings

$\{b[3:0], c[2:0]\}$

$\{b[3], b[2], b[1], b[0], c[2], c[1], c[0]\}$

$\{a, b[3:0], w, 3'b101\}$

$\{a, b[3], b[2], b[1], b[0], w, 1'b1, 1'b0, 1'b1\}$

$\{4\{w\}\}$

$\{w, w, w, w\}$

$\{b, \{3\{a, b\}\}\}$

$\{b, a, b, a, b, a, b\}$

Operators

Arithmetic Operators	+, -, *, /, %
Relational Operators	<, <=, >, >=
Equality Operators	==, !=, ===, !==
Logical Operators	!, &&,
Bit-Wise Operators	~, &, , ^, ~^
Unary Reduction	&, ~&, , ~ , ^, ~^
Shift Operators	>>, <<
Conditional Operators	?:
Concatenations	{ }

Operators (cont.)

- Example

opa = 0010

opb = 1100

opc = 0000

unary reduction

& opa = 0

0 & 0 & 1 & 0 = 0

logical operation

opa && opc = 0

opa = 0010 → true
opc = 0000 → false
true && false = false

bit-wise operation

opa & opb = 0000

$$\begin{array}{r} 0000 \\ \& 1100 \\ \hline 0000 \end{array}$$

bit-wise operation

~ opa = 1101

all bits are 0 → logic false

logical operation

opa && opb = 1

opa = 0010 → true
opb = 1100 → true
true && true = true

logical operation

! opa = 0

Compiler Directives

`define

- *`define* RAM_SIZE 16
- Defining a name and gives a constant value to it.

`include

- *`include* adder.v
- Including the entire contents of other verilog source file.

`timescale

- *`timescale* 100ns/1ns
- Setting the reference time unit and time precision of your simulation.

System Tasks

\$monitor

- *\$monitor* (\$time,"%d %d %d",address,sinout,cosout);
- Displays the values of the argument list whenever any of the arguments change except \$time.

\$display

- *\$display* ("%d %d %d",address,sinout,cosout);
- Prints out the current values of the signals in the argument list

\$finish

- *\$finish*
- Terminate the simulation

Gate Level Modeling

- Gate Level Modeling
- Case Study

Gate Level Modeling

Steps

- Develop the boolean function of output
- Draw the circuit with logic gates/primitives
- Connect gates/primitives with net (usually wire)

HDL: Hardware **Description** Language


- Figure out architecture first, then write code.

Primitives

- Primitives are modules ready to be instanced
- Smallest modeling block for simulator
- Verilog build-in primitive gate
 - and, or, not, buf, xor, nand, nor, xnor*
 - prim_name inst_name(output, in0, in1,....);*
- User defined primitive (UDP)
 - building block defined by designer

Case Study

1-bit Full Adder

 


Ci	A	B	Co	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Case Study

1-bit Full Adder
 
$$co = (a \cdot b) + (b \cdot ci) + (ci \cdot a);$$





```
30
31 module FA_co ( co, a, b, ci );
32
33     input    a, b, ci;
34     output   co;
35     wire     ab, bc, ca;
36
37     and g0( ab, a, b );
38     and g1( bc, b, c );
39     and g2( ca, c, a );
40     or  g3( co, ab, bc, ca );
41
42 endmodule
43
```

Case Study

1-bit Full Adder

$$\text{sum} = a \oplus b \oplus ci$$

  

```
44 module FA_sum ( sum, a, b, ci );  
45  
46     input  a, b, ci;  
47     output sum, co;  
48  
49     xor g1( sum, a, b, ci );  
50  
51 endmodule  
52
```


Case Study

1-bit Full Adder

Full Adder Connection

- Instance *ins_c* from FA_co
- Instance *ins_s* from FA_sum
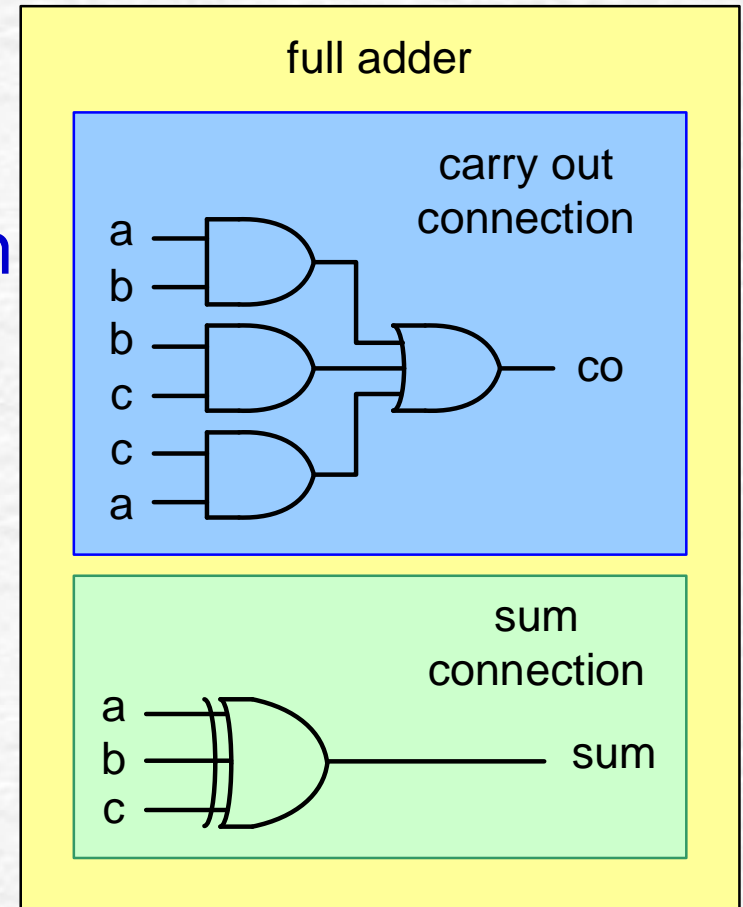
```
20
21 module FA_gatelevel( sum, co, a, b, ci );
22
23     input    a, b, ci;
24     output   sum, co;
25
26     FA_co    ins_c( co, a, b, ci );
27     FA_sum    ins_s( sum, a, b, ci );
28
29 endmodule
30
```



RT-Level & Behavioral Level Modeling


- RT-Level & Behavioral Level Modeling
- Case Study

RT-Level & Behavioral Level Modeling

- High level description
 - User friendly
 - Concise code
 - Faster simulation speed (event driven)
- Widely used for some common operations
 - $+$, $-$, $*$
 - $\&$, $|$, \sim
- Two main formats
 - always block (for behavior level)
 - assign (for RT level)

Case Study

1-bit Full Adder

 

$$\{Co, S\} = A + B + Ci$$

Case Study

1-bit Full Adder

- RT-level modeling of combinational circuit
 - Describe boolean function with *operators* and use continuous assignment *assign*

```
11
12 module FA_rtlevel( sum, co, a, b, ci );
13
14     input    a, b, ci;
15     output   sum, co;
16
17     assign   { co, sum } = a + b + ci;
18
19 endmodule
20
```

Case Study

1-bit Full Adder

Behavior-level modeling of combinational circuit:


- Use event-driven construct: **always** block
- Event: **@(*sensitive_list*)**

```
1
2 module FA_behavior( sum, co, a, b, ci );
3
4     input    a, b, ci;
5     output   sum, co;
6     reg      sum, co;
7
8     always@ ( a or b or ci )
9         { co, sum } = a + b + ci;
10
11 endmodule
12
```



Test bench

Test Methodology

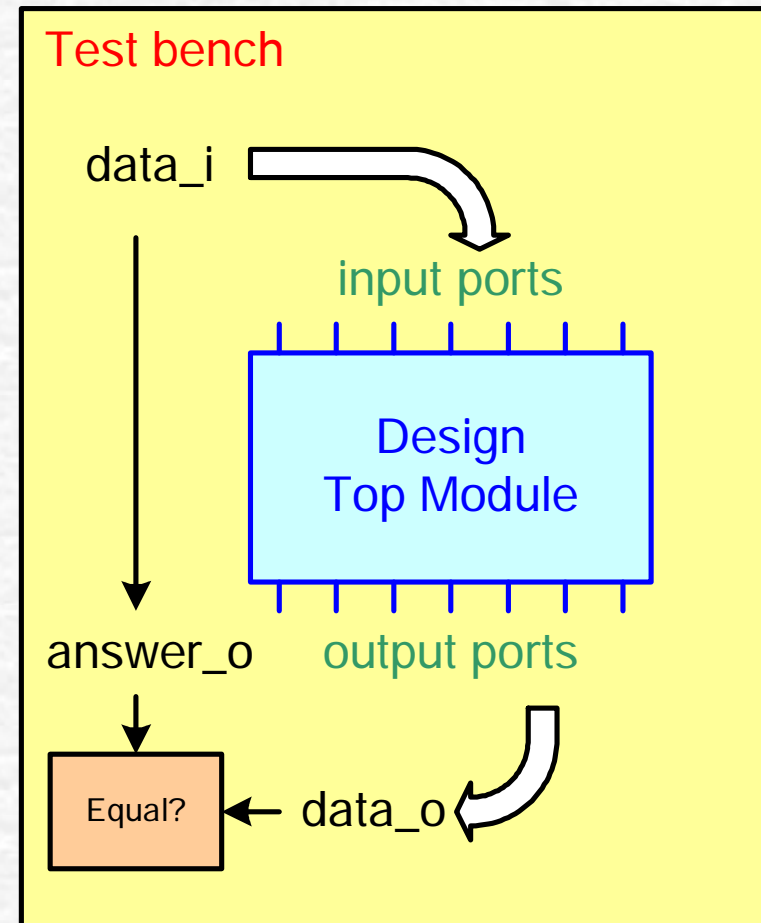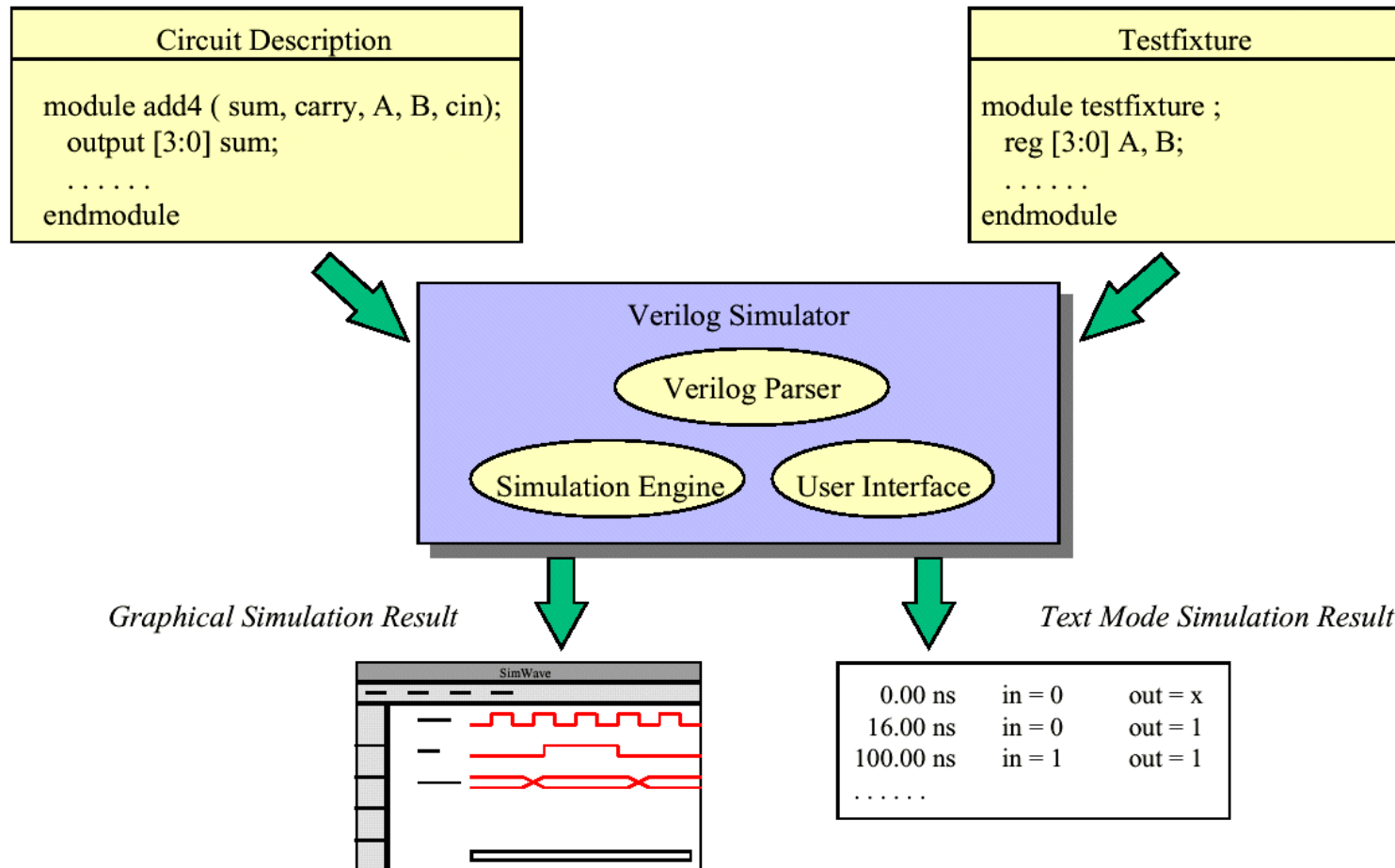- Systematically verify the functionality of a model.
- Simulation:
 - (1) detect syntax violations in source code
 - (2) simulate behavior
 - (3) monitor results



Verilog Simulator



Testbench for Full Adder

```
module t_full_add();  
  reg    a, b, cin;           // for stimulus waveforms  
  wire   sum, c_out;  
  
  full_add M1 (sum, c_out, a, b, cin); //DUT  
  
  initial #200 $finish;       // Stopwatch  
  
  initial begin               // Stimulus patterns  
    #10 a = 0; b = 0; cin = 0; // Statements execute in sequence  
    #10 a = 0; b = 1; cin = 0;  
    #10 a = 1; b = 0; cin = 0;  
    #10 a = 1; b = 1; cin = 0;  
    #10 a = 0; b = 0; cin = 1;  
    #10 a = 0; b = 1; cin = 1;  
    #10 a = 1; b = 0; cin = 1;  
    #10 a = 1; b = 1; cin = 1;  
  end  
endmodule
```


Summary

Design module

- Gate-level or RT-level
- Real hardware
 - Instance of modules exist all the time
- Each module has architecture figure
 - Plot architecture figures before you write verilog codes

Test bench

- Feed input data and compare output values versus time
- Usually behavior level
- Not real hardware, just like C/C++

Note

- Verilog is a platform
 - Support hardware design (design module)
 - Also support C/C++ like coding (test bench)
- How to write verilog well
 - Know basic concepts and syntax
 - Get a good reference (a person or some code files)
 - Form a good coding habit
 - Naming rule, comments, format partition (assign or always block)
- Hardware
 - Combinational circuits (today's topic)
 - 畫圖(architecture), then 連連看(coding)
 - Sequential circuits (we won't model them in this course)
 - register: element to store data